

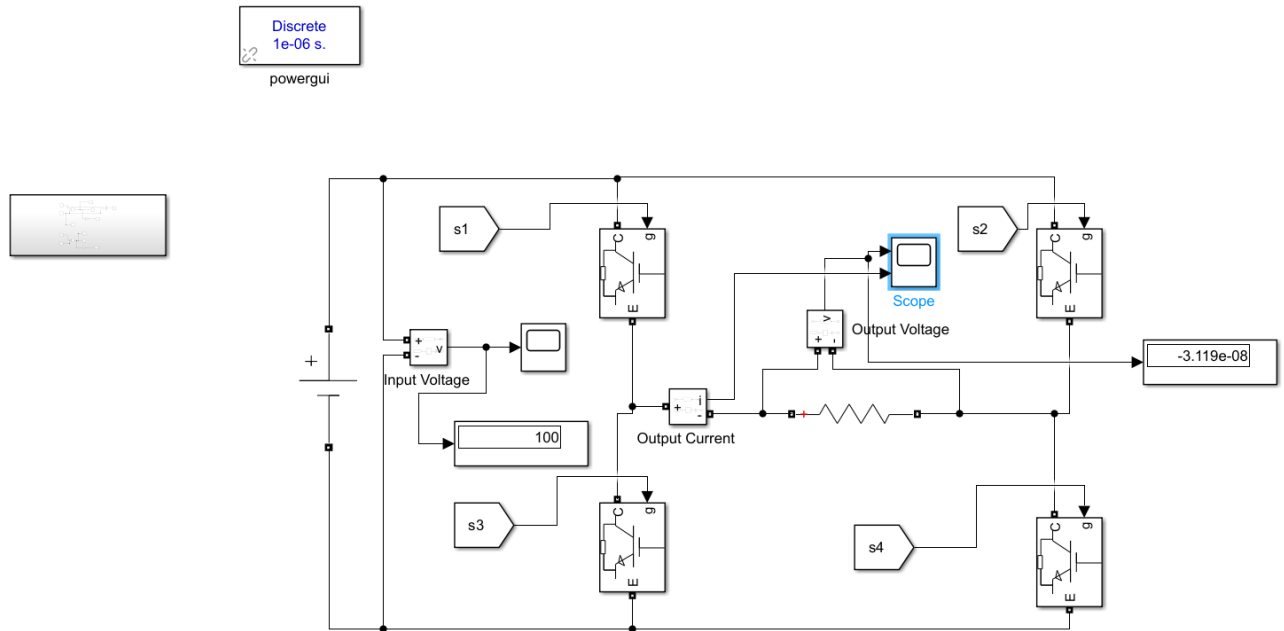





Project Report

Circuit Diagram (Bipolar) :-

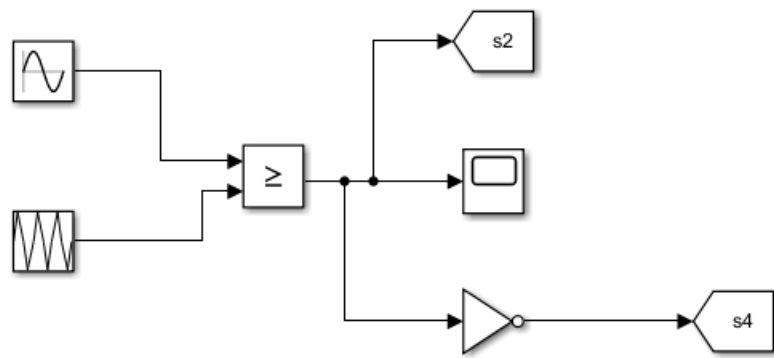


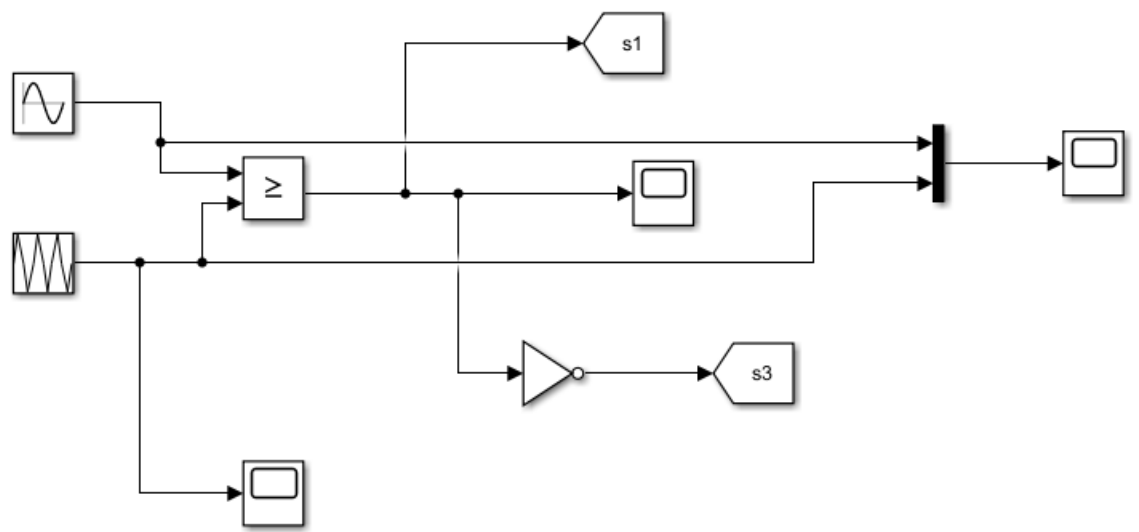


Output :-

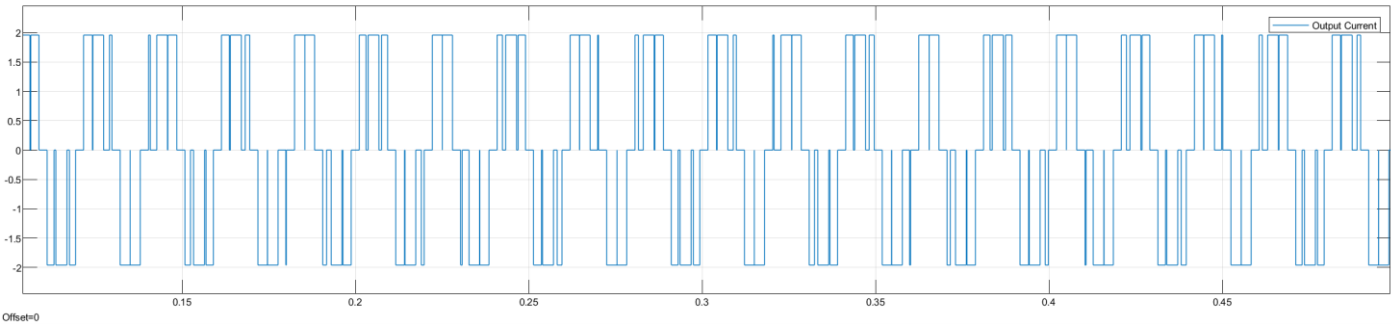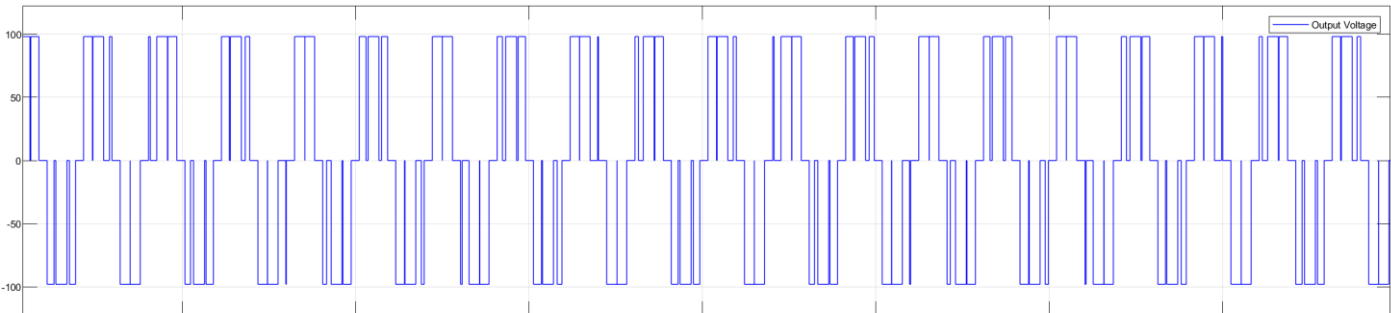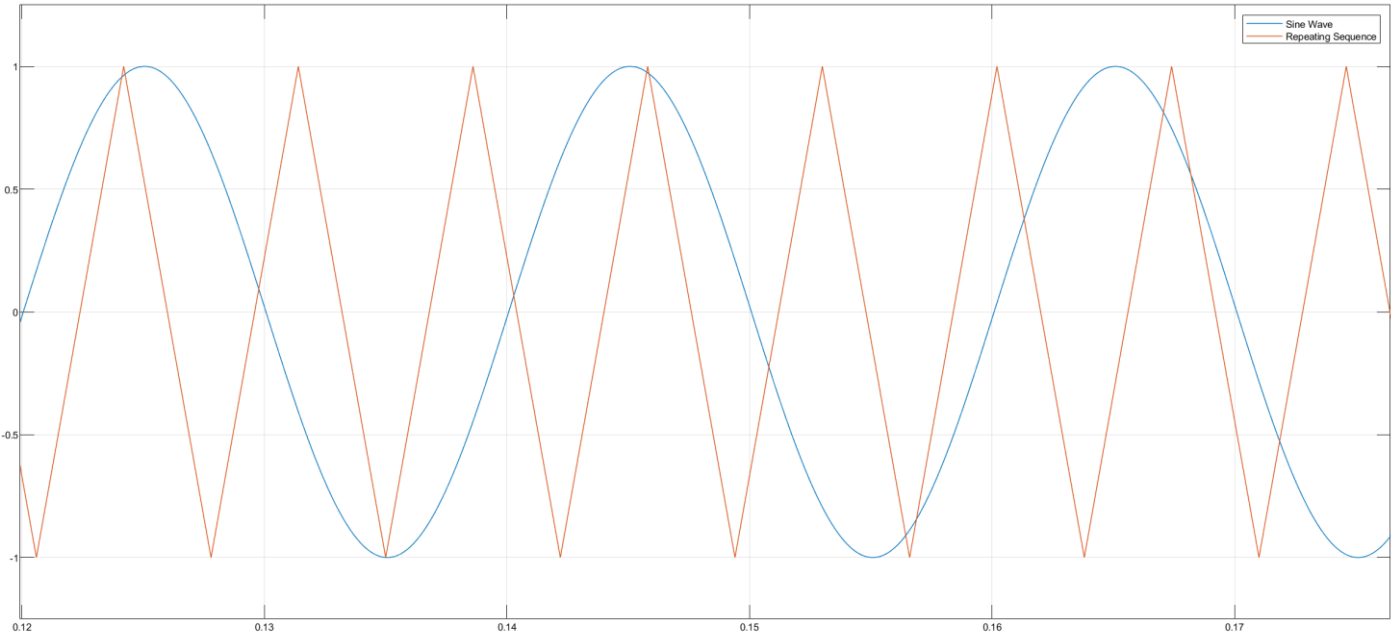



FFT :-

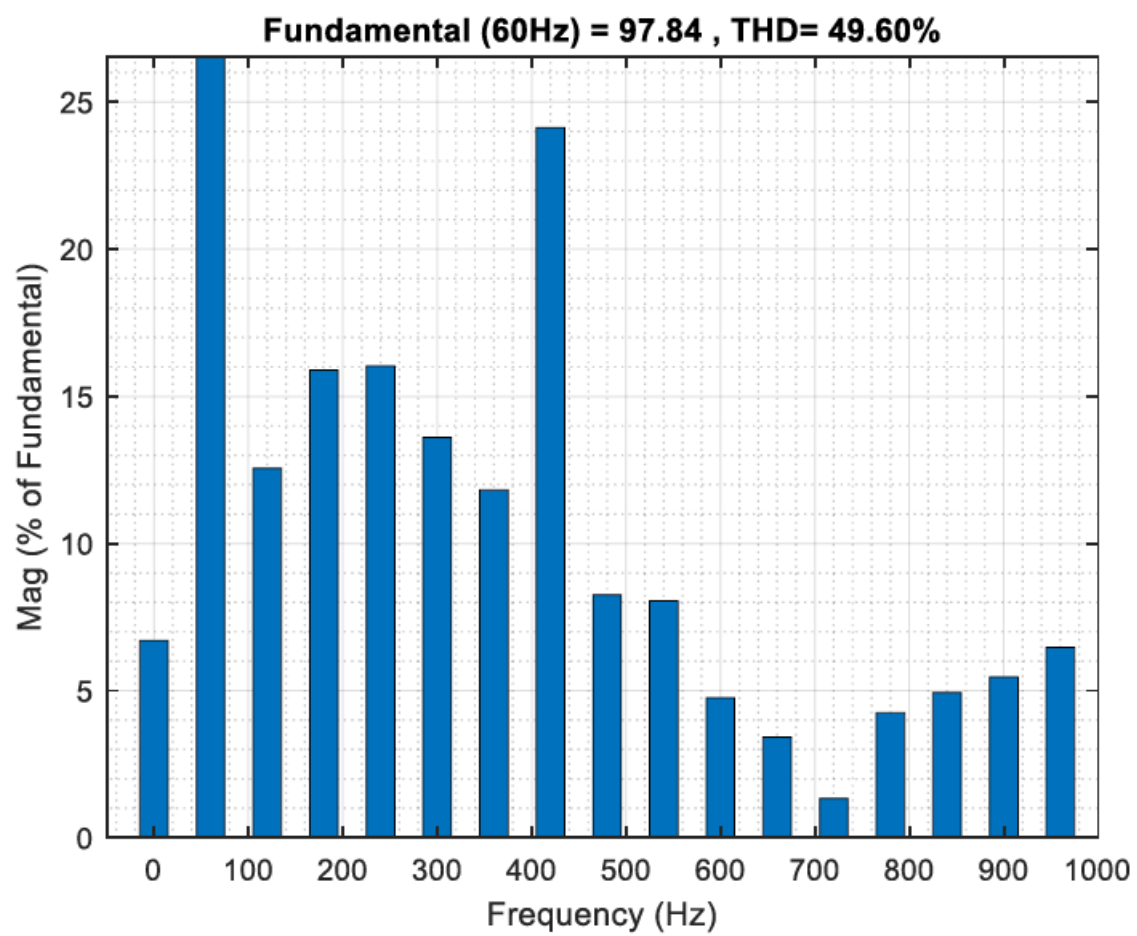


Circuit Diagram (unipolar) :-

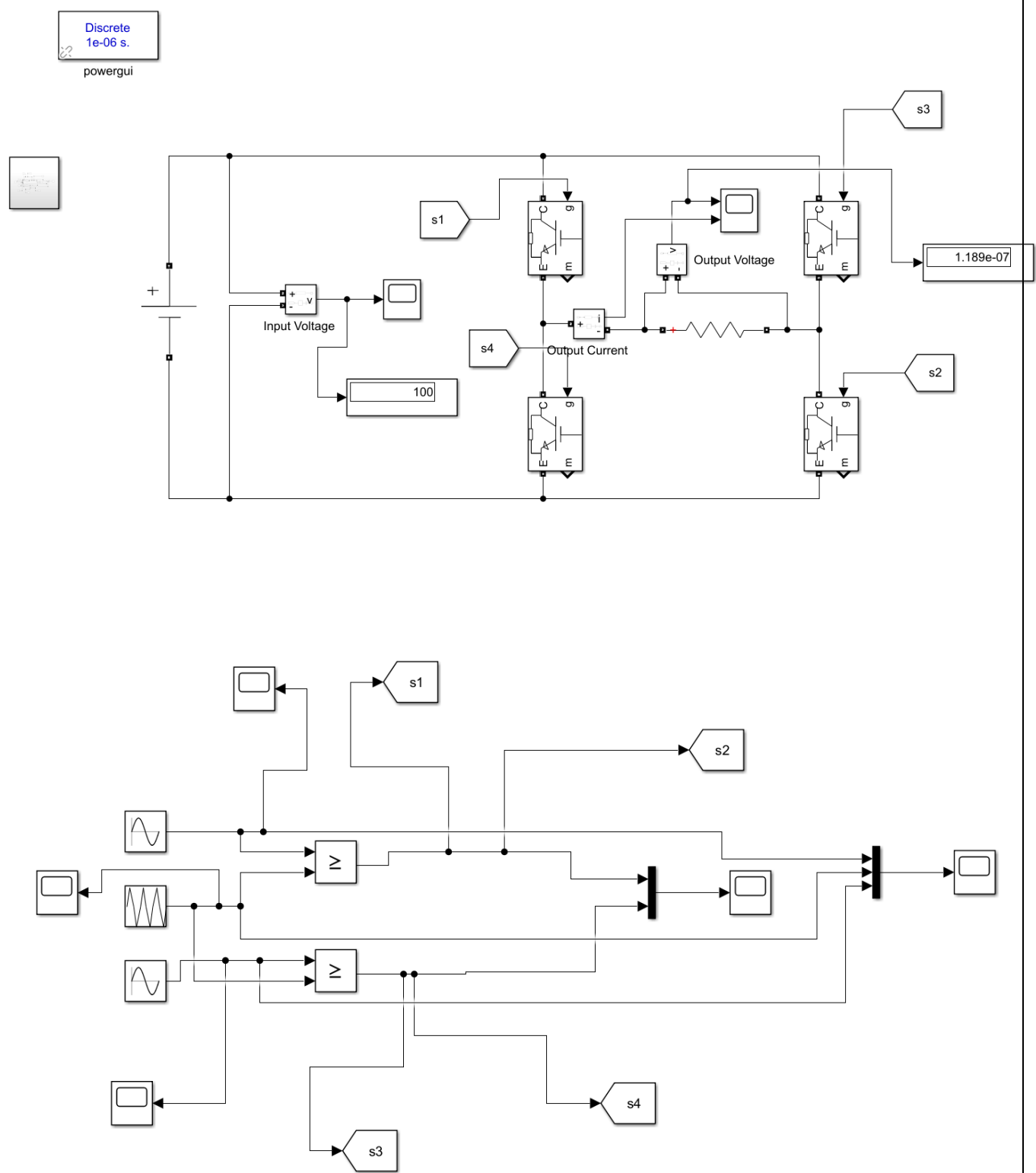

Output :-

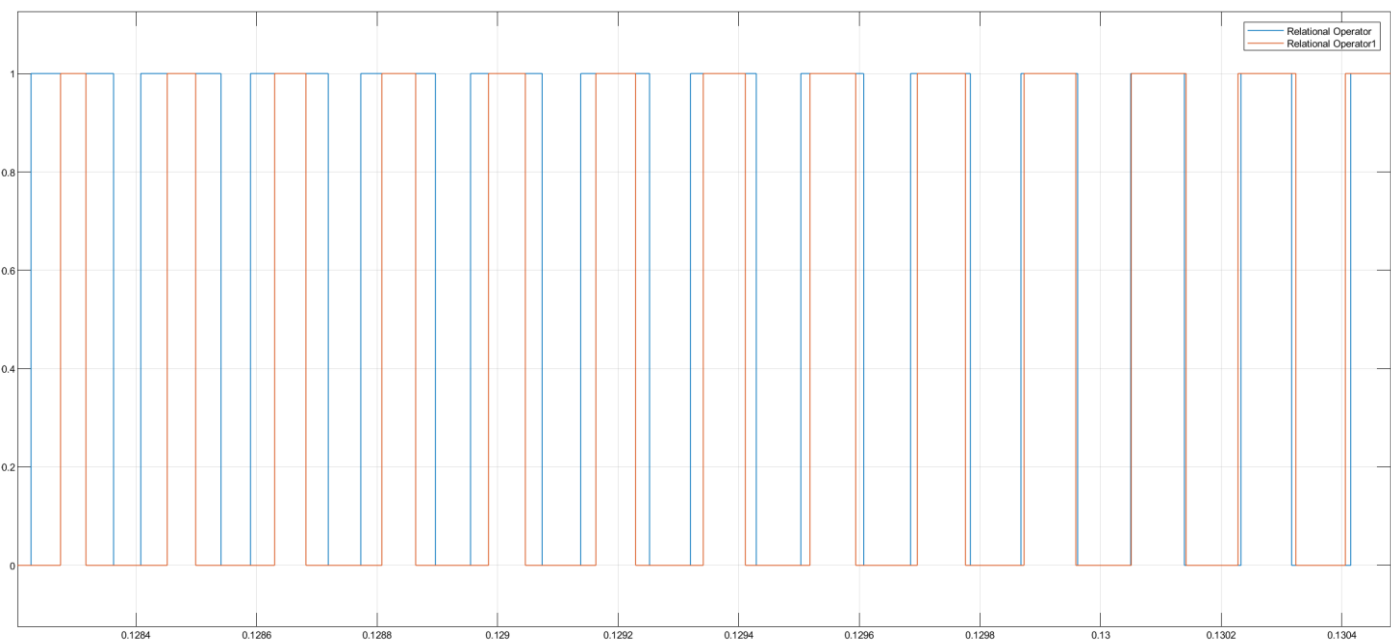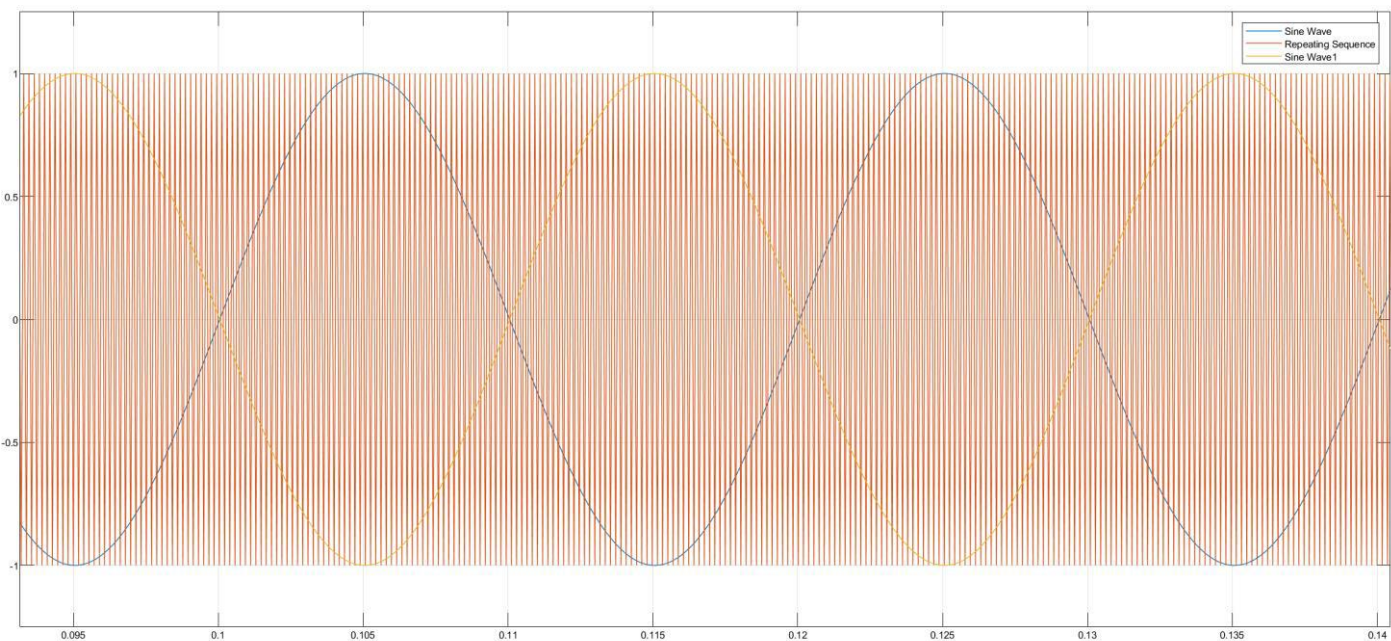

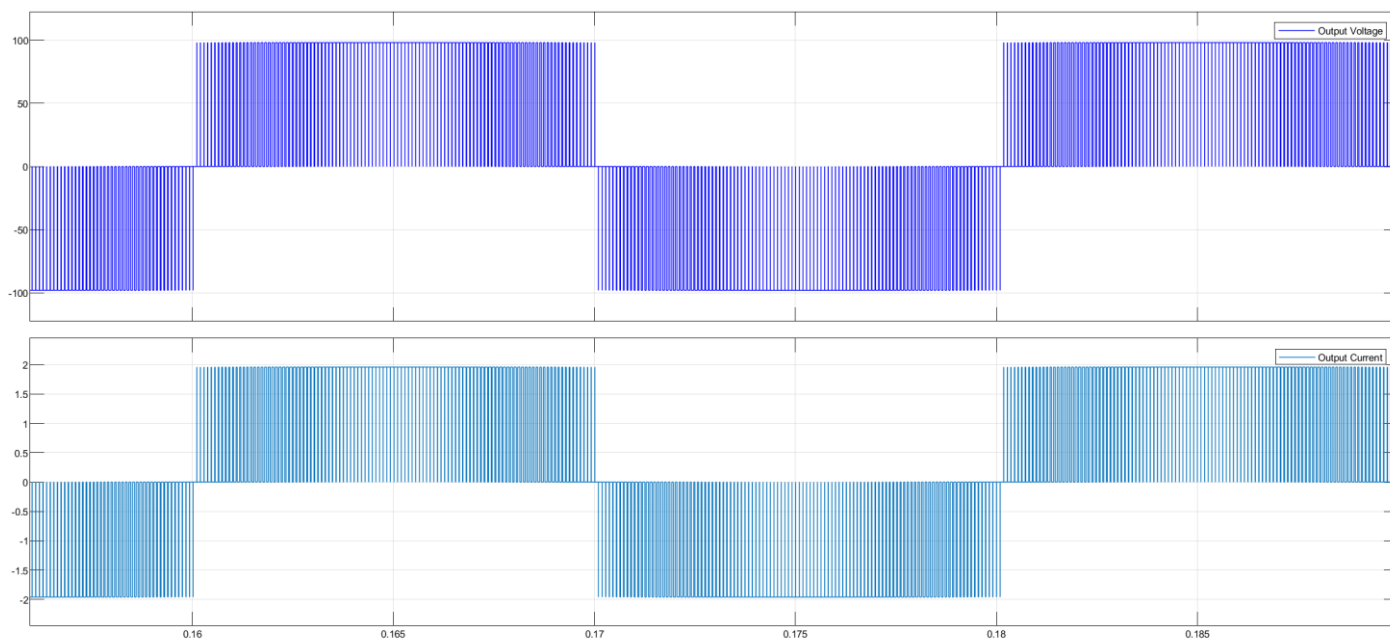

FFT :-

